

**Indian Maritime University**  
**(A Central University, Govt of India)**  
**End Semester Examinations – December 2023**  
**Programme Name: B.TECH.(NAOE)**  
**Semester: V**  
**Subject Code: UG12T2505**  
**Subject Name: Basic Electronics Engineering**

---

Date: 15.12.2023

Max Marks: 70

Duration: 03 Hrs

Pass Marks: 35

---

General Instructions

- (i) All Sections (A, B & C) are to be attempted.
- (ii) Options, if any, are specified in respective section.
- (iii) Scientific Calculator is permitted.

**Section A**

Ten MCQs/Fill in the Blanks of One Mark each – Choose the correct answer.  
Objective Questions (MCQ/True or False/Fill in the blanks/Match the following)  
10 X 1 = 10 Marks

- 1) Which among the following is a current controlled device
  - a) MOSFET
  - b) IGBT
  - c) BJT
  - d) JFET
  
- 2) Calculate the value of  $I_E$  in a transistor for which  $\beta = 50$ ,  $I_B = 20\mu A$ 
  - a) 1.02mA
  - b) 1.5mA
  - c) 2 mA
  - d) 3mA
  
- 3) The magnitude of current through a Zener diode in a Zener voltage regulator under full-load condition is
  - a) Maximum

- b) Zero
  - c) Remains constant irrespective of load
  - d) Minimum
- 4) In LC transistor oscillators the active component is used as
- a) Inductor
  - b) Capacitor
  - c) Resistor
  - d) Transistor
- 5) The minimum number of NAND gates required to design an AND gate.
- (a) 4
  - (b) 3
  - (c) 2
  - (d) 1
- 6) Why doping is required?
- (a) To decrease the conductivity of a pure or intrinsic semiconductor.
  - (b) To increase the conductivity of a pure or intrinsic semiconductor.
  - (c) To engineer a different form of semiconductor material with higher level of conductivity.
  - (d) Both (b) and (c)
- 7) The type of feedback used to design an oscillator is \_\_\_\_\_.
- (a) Negative
  - (b) Positive
  - (c) Both (a) & (b)
  - (d) None of these
- 8) If the frequency of a wave is 20 Hz, the time period is \_\_\_\_\_.
- (a) 0.2 sec
  - (b) 0.05 sec
  - (c) 2.0 sec
  - (d) 20.0 sec

- 9) A message signal of frequency 20 kHz and peak voltage of 20 volts is used to modulate a carrier signal of frequency 2 MHz and peak voltage of 40 volts. The value of modulation percentage is equal to \_\_\_\_\_.
- (a) 33 %
  - (b) 50 %
  - (c) 25 %
  - (d) 75 %
- 10) Consider the following statements for a Bipolar Junction Transistor.
- 1.It is a current controlled device.
  - 2.It is made up of three different types of semiconductor materials.
  - 3.Both the majority and minority carriers participate in the conduction process.
  - 4.The minority current component is dependent upon temperature.

Which of these statement(s) is(are) correct?

- (a) 1, 2, 3 and 4
- (b) 2, 3 and 4
- (c) 1, 3 and 4
- (d) 1, 2 and 3

### **Section B**

Five Short Answer type Questions of Two marks each.

5 X 2 = 10 Marks

- 11. What are the three different configurations in transistor biasing?
- 12. Draw the circuit diagram and truth table of S-R Flip-flop mentioning the remark of each states?
- 13. State the Barkhausen's criteria for oscillation?
- 14. What is Modulation? Mention any two major requirements of it?
- 15. Why the base region of a BJT is lightly doped and collector region has the largest area?

### Section C


Seven Long Answer type Questions of Two marks each. Answer any Five.

10 X 5 = 50 Marks

16. Define shift register and explain the following two types of shift register with clock diagrams  
 (a) 4 bit Serial-in serial out (SISO) [5M]  
 (b) 4 bit Parallel-in serial out (PISO) [5M]

17. Explain the functioning of Wien-bridge oscillator with neat circuit diagram.

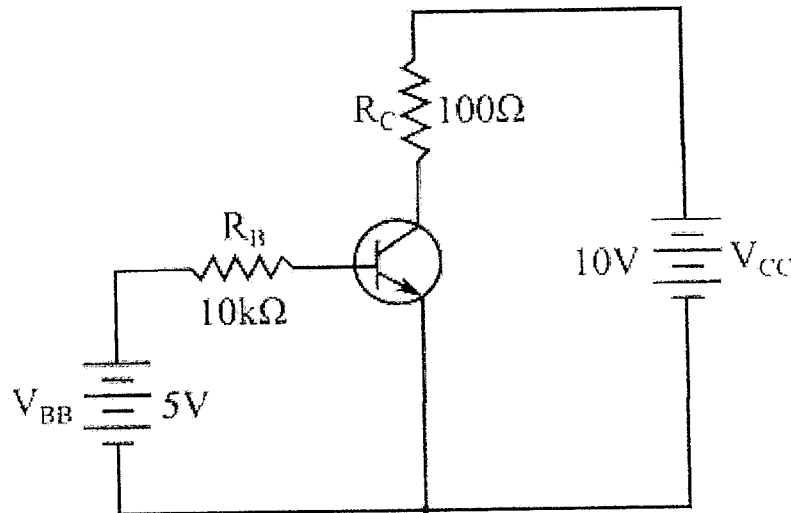18. (i) Determine the value of  $V_{CB}$  in the transistor circuit shown in the figure given below. The transistor is of Silicon and has  $\beta = 150$ .



(5 marks)

18. (ii) Simplify the boolean expression  $Y = \overline{A \cdot \overline{B} \cdot (A + C)} + \overline{A} \cdot B \cdot (A + B + \overline{C})$  and implement the simplified expression using logic circuit diagram.

(3+2 marks)

19. Draw and explain 3-bit Binary Weighted Resistor Digital-to-Analog (DAC) converter.

20. (i) An AM wave is represented by the expression:

$$v(t) = 5[1 + 0.6\cos(6280t)]\cos(62800t)$$

Evaluate the following: [5M]

- (a) What are the minimum and maximum amplitudes of the AM wave?
- (b) What frequency components are contained in the modulated wave and what is the peak amplitude of each component?
- (c) Modulation Index
- (d) Carrier Power, Side Band Power, and Total Power
- (e) Efficiency

20. (ii) Convert  $(123.125)_{10}$  to Base-2, Base-8, Base-16. [5M]

21. Design a 3-bit asynchronous UP/DOWN counter.

22. Explain the process of generating Amplitude Modulated Wave using the Square Law Modulator.